

# RoboJackets Electrical Training Week 0 Worksheet

Alex Xu  
Joe Spall

September 11, 2018  
v1.1

## Contents

<b>1</b>	<b>What is this worksheet? What's so special about it? Why should you read it?</b>	<b>2</b>
<b>2</b>	<b>Intro to Electricity</b>	<b>2</b>
<b>3</b>	<b>Capacitors and Inductors</b>	<b>3</b>
3.1	Capacitors . . . . .	3
3.2	Inductors . . . . .	3
<b>4</b>	<b>Diodes and FETs</b>	<b>3</b>
<b>5</b>	<b>Circuit Analysis</b>	<b>4</b>
5.1	Parallel and Series . . . . .	4
5.2	Kirchoff's Law . . . . .	4
<b>6</b>	<b>Prototyping</b>	<b>5</b>

# 1 What is this worksheet? What's so special about it? Why should you read it?

There are three documents in the Week 0 training: a worksheet, its answer sheet and an informational sheet that explains everything in this document. This document is the worksheet.

RoboJackets build robots, and we are going to help you understand how we built them so you can do it as well. The electrical training focuses on the idea of “Prototyping”, which requires a basic understanding of electricity. We therefore prepared Week 0 session for those have little knowledge in electricity so you'll walk in to Week 1 less confused.

This worksheet contains all **a variety questions pertaining to information you should know when you walk into Week 1** electrical training session. It is perfectly fine if you do not know certain, or any, concepts covered in this worksheet. If there are any concepts in this worksheet you do not feel comfortable with, please ask any of the instructors or your classmates for help. For more background on the topics, you can also refer to the Informational Sheet. Please only refer to the Answer Sheet after you have attempted to answer all of the questions.

## 2 Intro to Electricity

1. Resistance is measured in \_\_\_\_\_. (Unit)
2. If the two terminals of a resistor are measured to be -3.3V and -5V with reference to some arbitrary pre-defined ground. The potential difference across the resistor is \_\_\_\_\_.
3. To measure current, an Ammeter is connected in \_\_\_\_\_ (parallel / series) with the desired path. To measure voltage, a Voltmeter is connected in \_\_\_\_\_ (parallel / series) with the desired path.
4. 5V is applied across a resistor and the resultant current is 0.2A. The resistance across the resistor is \_\_\_\_\_.
5. The resistor in the previous question is dissipating energy at \_\_\_\_\_W.
6. With reference to the color coding diagram (Figure 1), a resistor of yellow, violet, brown and gold color code has a resistance of \_\_\_\_\_.

Color	Digit value	Multiplier	Multiplied Out	Tolerance
Black	0	$10^0$	1	
Brown	1	$10^1$	10	
Red	2	$10^2$	100	
Orange	3	$10^3$	1,000	
Yellow	4	$10^4$	10,000	
Green	5	$10^5$	100,000	
Blue	6	$10^6$	1,000,000	
Violet	7	$10^7$	10,000,000	
Gray	8	$10^8$	100,000,000	
White	9	$10^9$	1,000,000,000	
Gold				±5%
Silver				±10%

Figure 1: Resistor Coding Chart

## 3 Capacitors and Inductors

### 3.1 Capacitors

1. Capacitors are measured in \_\_\_\_\_. (Unit)
2. 0.0025 coulomb of charge accumulates across a capacitor when 5V is applied, its capacitance is \_\_\_\_\_.
3. There are two types of capacitors: ceramic and electrolytic. Both of them do not have polarity (True / False).
4. Electrolytic capacitors usually have a lower value than ceramic capacitors. (True / False)
5. Capacitors are used in circuits for what purposes related to power?

### 3.2 Inductors

1. Inductors are measured in \_\_\_\_\_. (Unit)
2. Inductors can typically be found in electro-mechanical parts on a robot. (True / False)
3. An ohmmeter is connected across an inductor and the meter reads zero ohms. The inductor is definitely broken. (True / False)

## 4 Diodes and FETs

1. LEDs are a type of diode, and they're very delicate. We need to apply additional resistors in series to an LED to prevent too much current. If the supply voltage is 5V and the LED is rated at 20mA maximum, what's the minimum resistance of the additional resistor?
2. FETs are used to help low voltage logic circuits to control high voltage and current-drawing motors. (True / False)
3. For the Figure 2, assume the two transistors are functioning properly with respect to Vdd and Vss levels. What's the voltage level of Q when voltage at A equals Vdd?

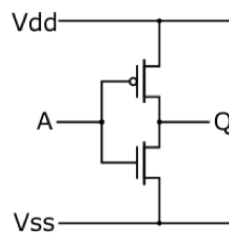


Figure 2: Transistor Operation Schematics

## 5 Circuit Analysis

### 5.1 Parallel and Series

1. Two  $1.2k\Omega$  resistors are in series, and this combination is in parallel with a  $3.3k\Omega$  resistor (left circuit in Figure 3). The total resistance is \_\_\_\_\_.
2. Consider the right circuit in Figure 3. Assume ECHO\_5V is actually 5V. What's the voltage at ECHO\_OUT?
3. A  $10\mu F$ ,  $20\mu F$ ,  $22\mu F$ , and  $100\mu F$  capacitor are in parallel. The total capacitance is \_\_\_\_\_.
4. Now the capacitors in Q3 are in series. Their capacitance is \_\_\_\_\_.

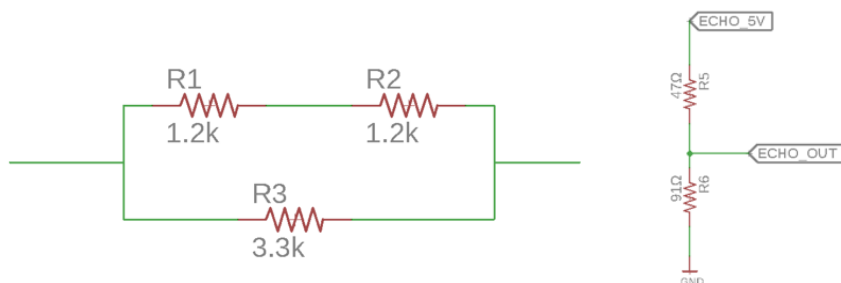


Figure 3: Parallel and Series Analysis

### 5.2 Kirchoff's Law

1. In Figure 4,  $R_1 = 4\Omega$ ,  $R_2 = 3\Omega$ ,  $R_3 = 2\Omega$ ,  $\varepsilon_1 = 12V$ ,  $\varepsilon_2 = 8V$ . What's the current through  $R_2$ .

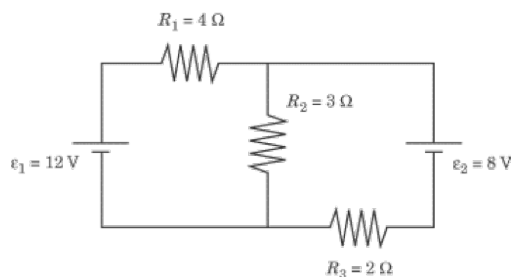


Figure 4: Kirchoff's Circuit Analysis

## 6 Prototyping

1. Breadboards are very useful during prototyping. If the breadboard in front of you is oriented so that the longer side faces you (see Figure 5). Holes in the same rows are \_\_\_\_\_ and those in the same column are \_\_\_\_\_. Columns on the two sides of the middle trench are \_\_\_\_\_ (Fill in with Connected or Not connected).
2. When prototyping with breadboard, you should use \_\_\_\_\_ (single-core / multi-core) for a signal line. When crimping a multi-core wire, one (should / should not) twist the wire to make it more solid.
3. Is R1 in the right-sided circuit of Figure 5 acting as a pull-down resistor or pull-up resistor? What does it do?

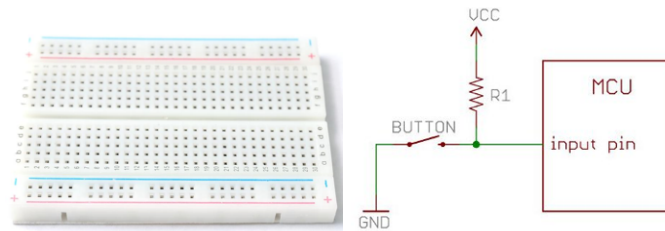


Figure 5: Example breadboard and pull-up resistor network

4. Fuse is the most fragile part of your circuit. Replace it with a wire to make your circuit more robust (True / False).